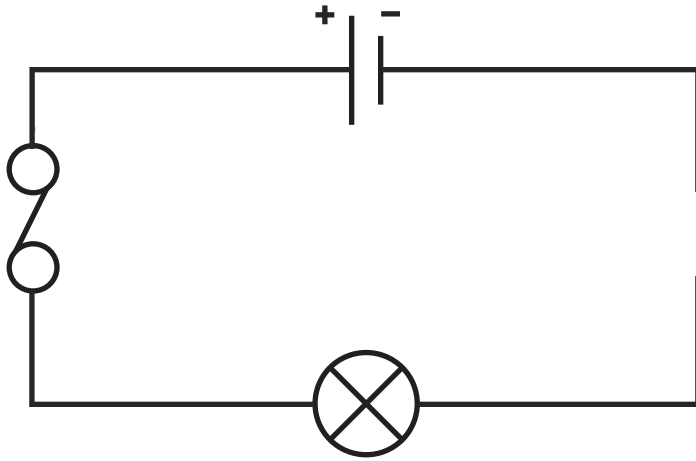



Find the Problem With the Electrical Circuit

1




Find the Problem With the Electrical Circuit

2

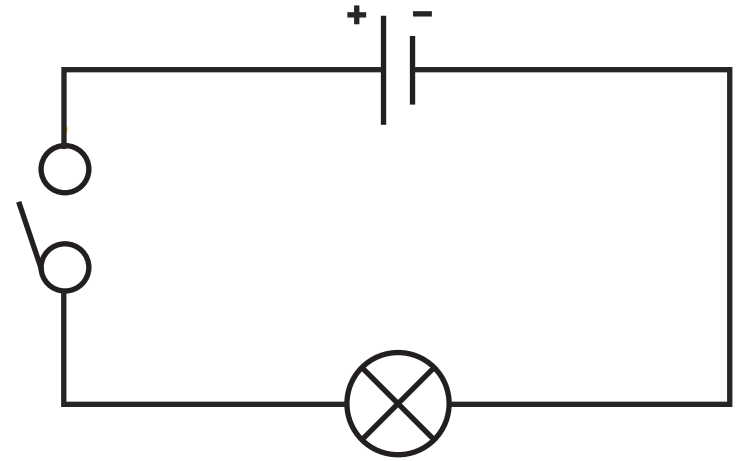


Find the Problem With the Electrical Circuit

3

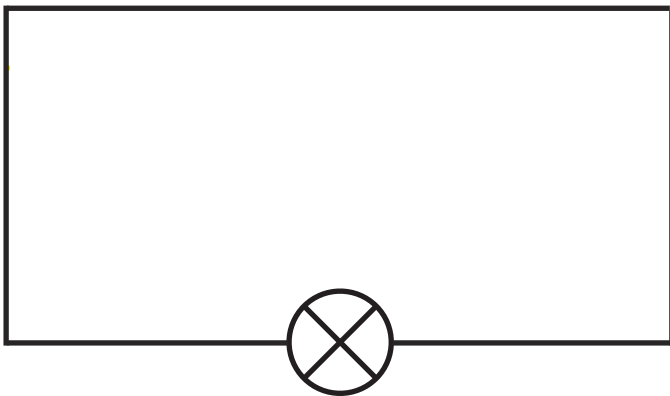


Find the Problem With the Electrical Circuit

4

 


Find the Problem With the Electrical Circuit

5

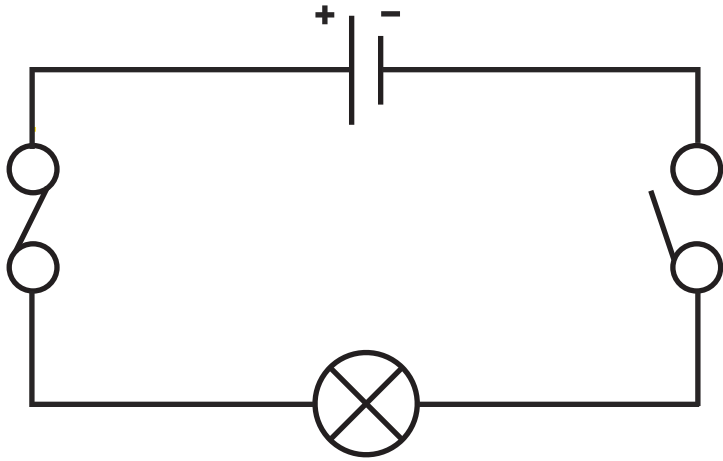


Find the Problem With the Electrical Circuit

6

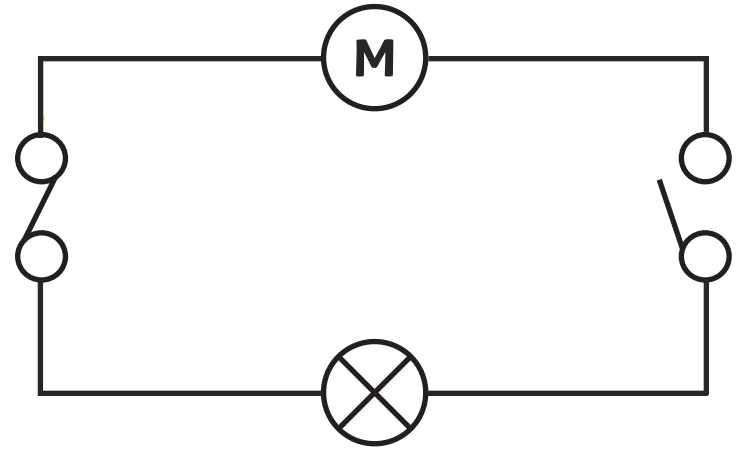


Find the Problem With the Electrical Circuit **Answer Key**

1

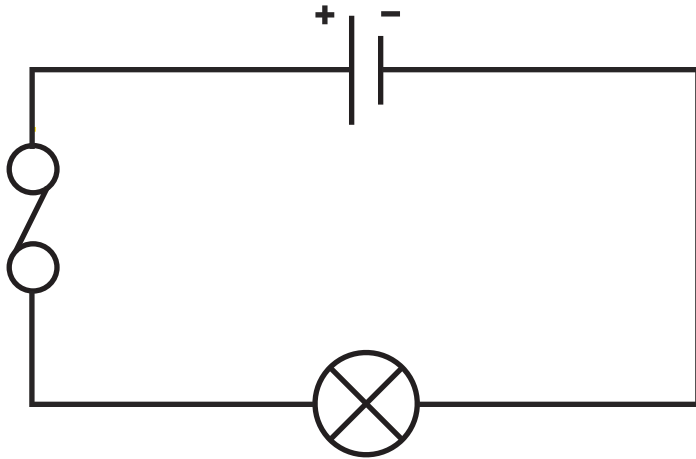


Find the Problem With the Electrical Circuit **Answer Key**

2

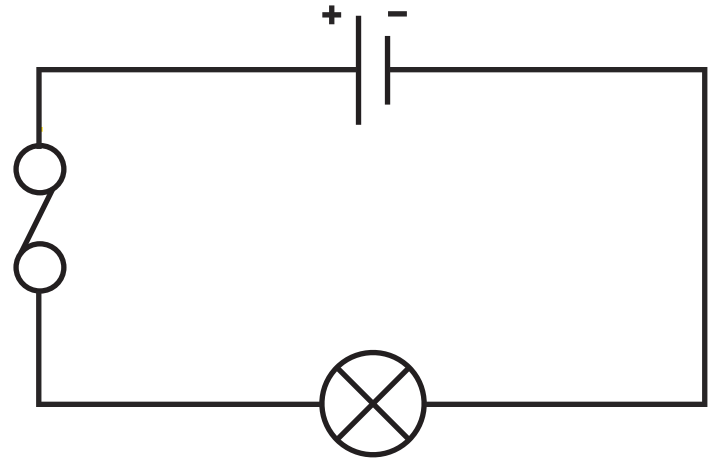


Find the Problem With the Electrical Circuit **Answer Key**

3

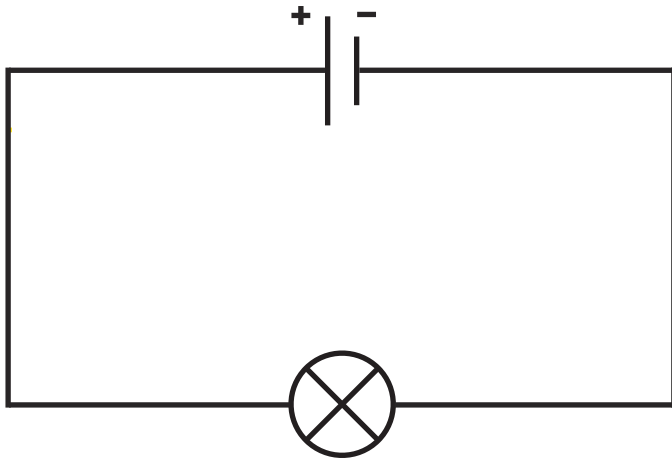


Find the Problem With the Electrical Circuit **Answer Key**

4

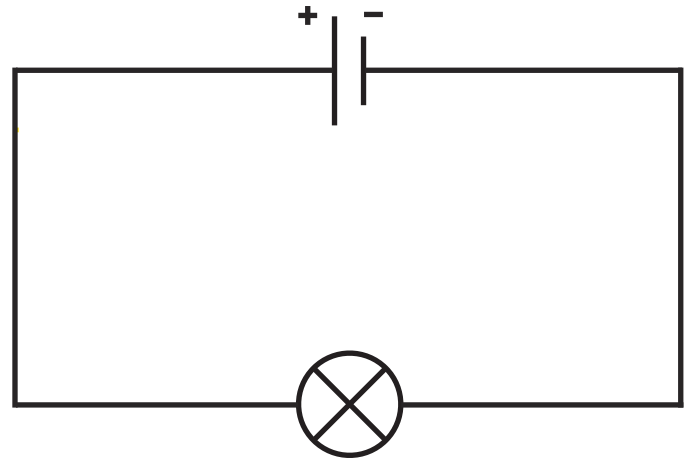

Find the Problem With the Electrical Circuit **Answer Key**

5

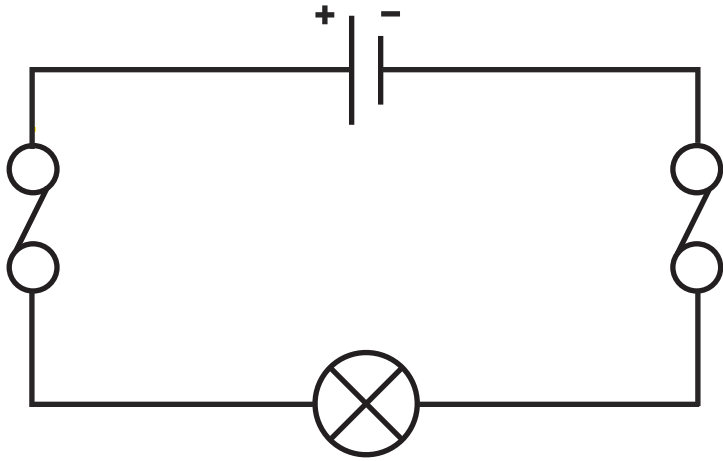

Find the Problem With the Electrical Circuit **Answer Key**

6

