

# 4.2 Electrical Quantities

## Question Paper

Course	CIE IGCSE Physics
Section	4. Electricity & Magnetism
Topic	4.2 Electrical Quantities
Difficulty	Hard

**Time allowed:** 20  
**Score:** /9  
**Percentage:** /100

### Question 1


What is the definition of an electric field?

- A. A region in space in which a mass experiences a force due to the Earth's mass.
- B. A region in space through which electromagnetic radiation is passing.
- C. A region in space in which a compass needle experiences a force.
- D. A region in space in which an electric charge experiences a force.

[1 mark]
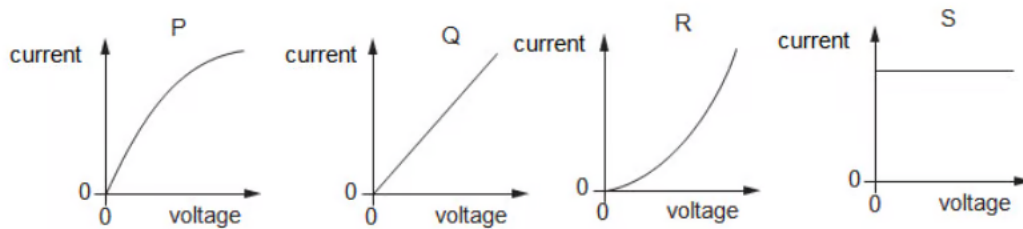
### Question 2

Four current-voltage graphs are given below.



One of them is for an ohmic resistor, and another is for a filament lamp.


Which is which?

	Filament lamp	Ohmic resistor
<b>A</b>	Q	S
<b>B</b>	R	Q
<b>C</b>	P	Q
<b>D</b>	Q	R

[1 mark]
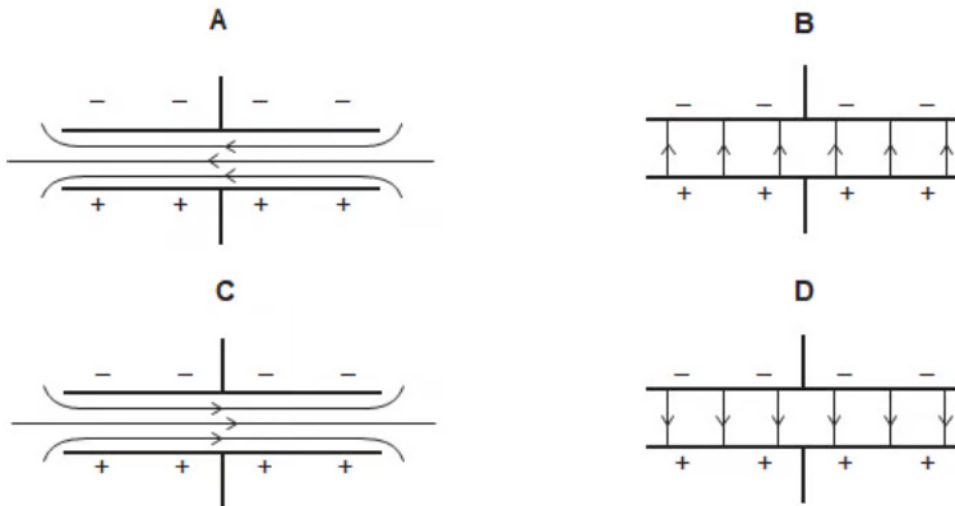
### Question 3

Which of the diagrams below shows the correct electric field pattern for oppositely charged parallel plates?



[1 mark]

### Question 4


Which row in the table gives the correct units for charge and for EMF?

	Charge	EMF
<b>A</b>	Q	E
<b>B</b>	C	V
<b>C</b>	A	J
<b>D</b>	J	$\equiv$

[1 mark]
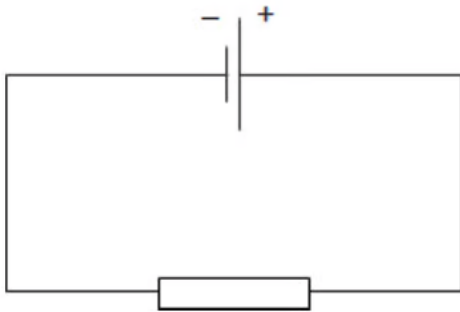
### Question 5

A student sets up a circuit as shown in the diagram



A charge of  $4.9\text{ C}$  flows through the lamp in  $0.7\text{ s}$ .

What is the current through the resistor, which direction do electrons flow through the resistor, and what is the direction of the conventional current through the resistor?

	current / A	direction of electron flow	direction of conventional current
<b>A</b>	7.00	Left to right	Right to left
<b>B</b>	3.43	Left to right	Right to left
<b>C</b>	7.00	Right to left	Right to left
<b>D</b>	3.43	Right to left	Right to left

[1 mark]

### Question 6

A student connects a  $6\text{ V}$  power supply to a  $3\ \Omega$  resistor. The resistor is left connected to the power supply for 1 minute.


How much power is dissipated by the resistor?

- A.  $2\text{ W}$
- B.  $12\text{ W}$
- C.  $720\text{ J}$
- D.  $18\text{ W}$

[1 mark]
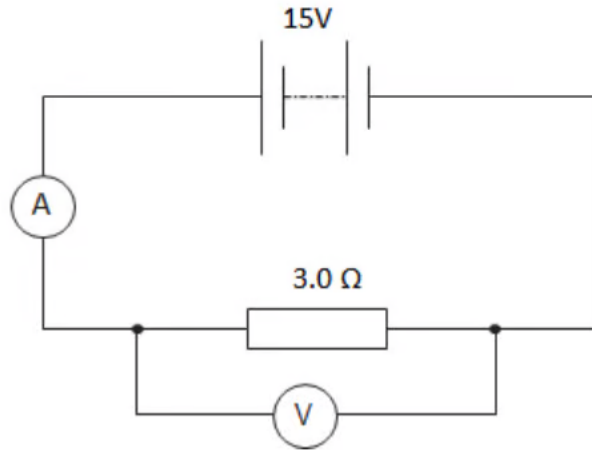
### Question 7

A  $3.0 \Omega$  resistor is connected to a 15 V power supply as shown in the diagram. The ammeter reads 5 A throughout the experiment.




How much energy is dissipated as heat by the resistor in 2 minutes?

- A. 9.0 kJ
- B. 150 J
- C. 600 J
- D. 5 J

[1 mark]

Question 8

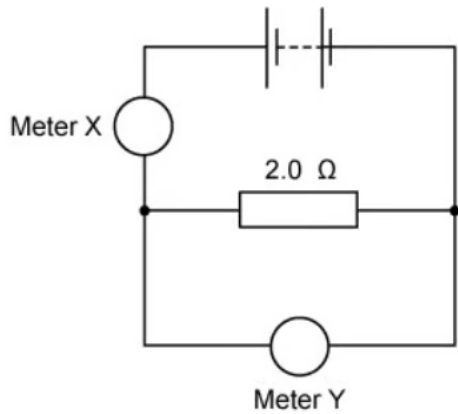

Which row in the table shows possible values for the two meters shown in the circuit diagram?

	X	Y
<b>A</b>	4.0	8.0
<b>B</b>	2.0	2.0
<b>C</b>	4.0	2.0
<b>D</b>	1.0	1.0

[1 mark]

Question 9

A student wants to measure the power dissipated by a  $10\text{ k}\Omega$  resistor.

She (obviously) knows the resistance of the resistor. What other equipment is **the minimum** required to determine the power dissipated?

- A. A voltmeter and an ammeter
- B. A voltmeter, an ammeter and a stopwatch
- C. A voltmeter only
- D. An ammeter and a stopwatch

[1 mark]