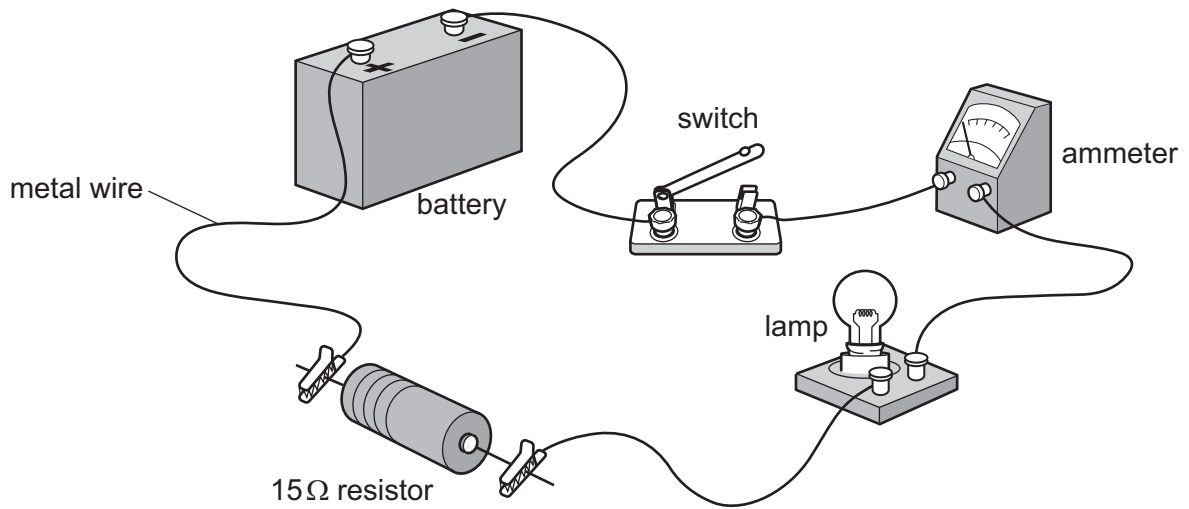


- 1 The diagram shows an electric circuit set up by a student.




When the switch is closed there is a current in the circuit.

State the name of the particles flowing in the metal wire.

..... [1]

[Total: 1]

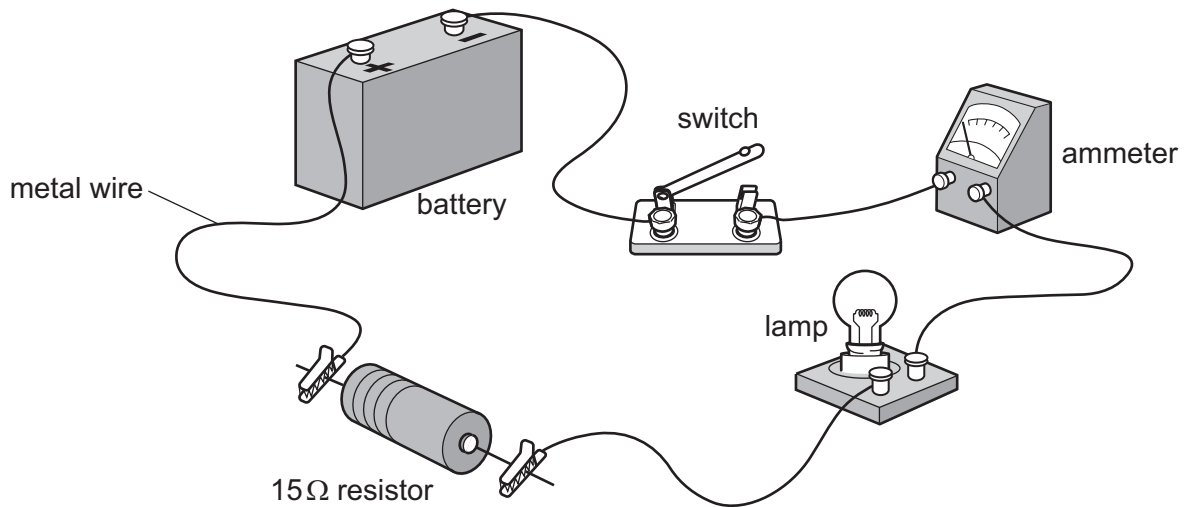2 The diagram shows an electric circuit set up by a student.



The current in the $15\ \Omega$ resistor in the diagram is $0.40\ \text{A}$ when the switch is closed.

Calculate the potential difference (p.d.) across the $15\ \Omega$ resistor.

p.d. across resistor = V [3]


[Total: 3]

3 A battery consists of four cells, each of e.m.f. $1.2\ \text{V}$, in series.

(a) Calculate the e.m.f. of the battery.

e.m.f. = [1]

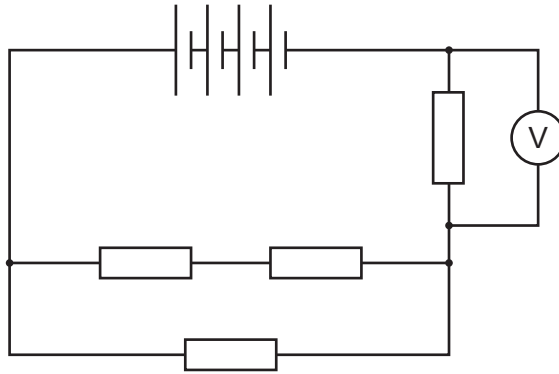(b) The battery is connected in a circuit with four $12\ \Omega$ resistors as shown in the circuit diagram.



Calculate the total resistance of this arrangement of resistors.

resistance = [3]

(c) Calculate the reading on the voltmeter in the circuit diagram.

reading = [2]

[Total: 6]